



EXPERIMENT – 2.3

NAME: UID:

SEMESTER: CLASS/GROUP:

D.O.P: SUBJECT CODE – 21ELH-101

Aim: To design simple DC motor control circuit.

Apparatus: ARDUINO UNO, DC motor, L293D, connecting wires.potentiometer.

Circuit Diagram:

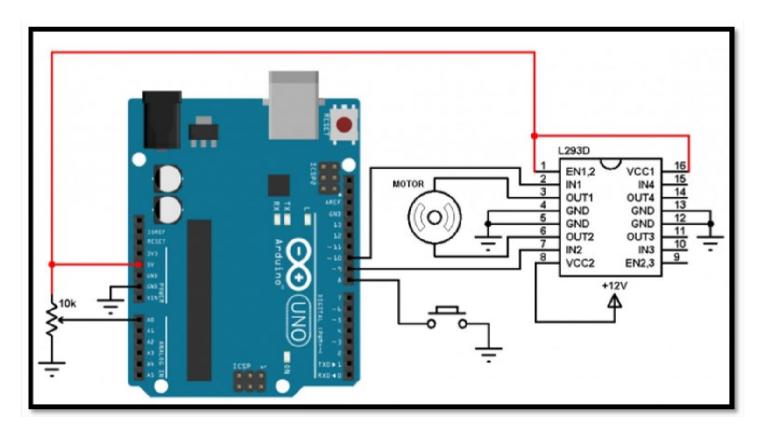






Fig.1 DC Motor Circuit

void loop() {


```
Program:
#define button 8
#define pot 0
#define pwm1
                 9
#define pwm2 10
boolean motor_dir = 0;int motor_speed;
void setup() {
pinMode(button, INPUT_PULLUP); pinMode(pwm1, OUTPUT); pinMode(pwm2, OUTPUT);
```



```
motor_speed = analogRead(pot) / 4; if(motor_dir)
analogWrite(pwm1, motor_speed);else
analogWrite(pwm2, motor_speed);
if(!digitalRead(button)){ // If direction button is pressed while(!digitalRead(button));
      // Wait until direction button released motor_dir = !motor_dir;
                                                                            // Toggle direction
variable if(motor_dir)
digitalWrite(pwm2, 0); else digitalWrite(pwm1, 0);
```






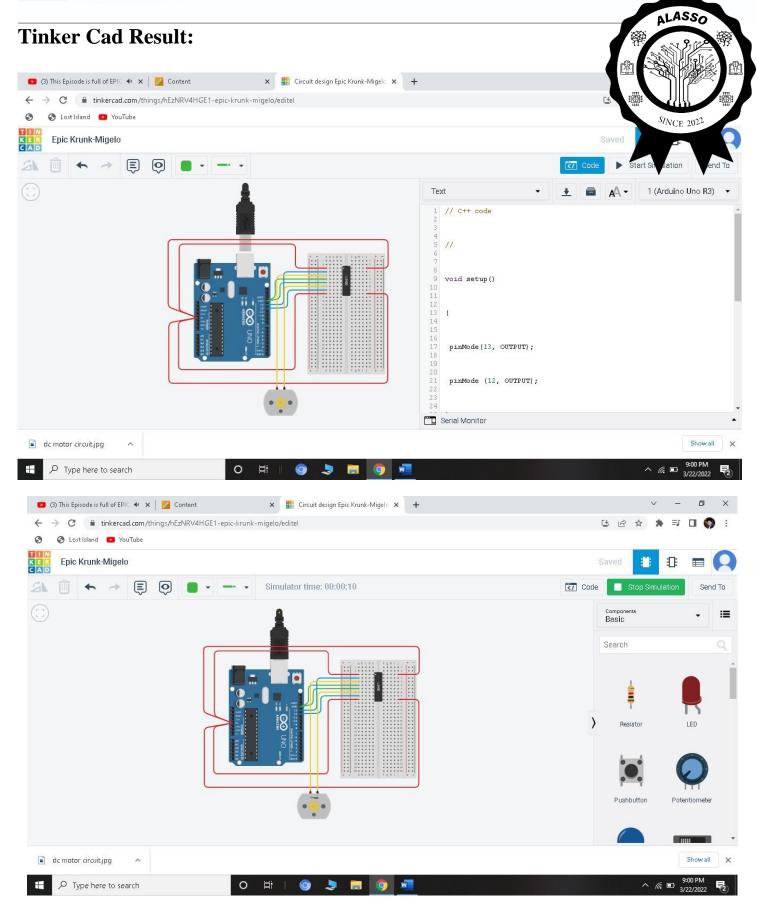





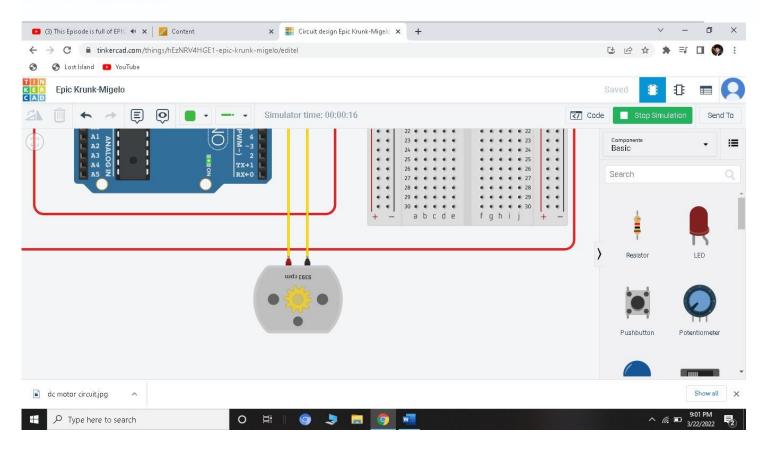


When 13 is High; 12 is Low







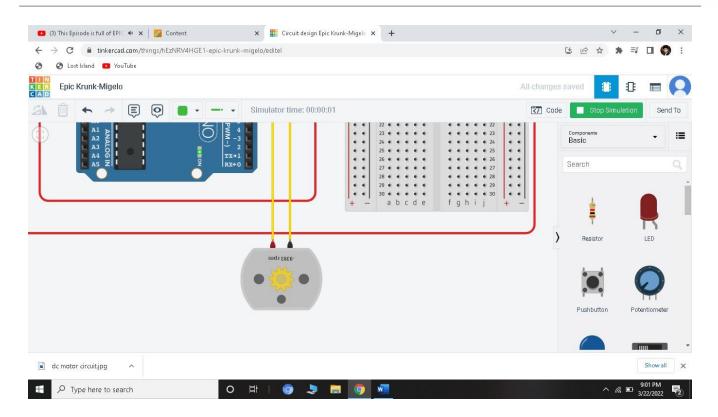

When 12 is High; 13 is Low

Result:

Designing of simple DC motor control circuit using Arduino is verified after uploading the program.

Evaluation Grid:

Sr. No.	Parameters	Marks Obtained	Maximum Marks
1.	Worksheet completion including		10
	writinglearning objectives/Outcomes.		
	(To be submitted at the end of the		
	day).		
2.	Post Lab Quiz Result.		5
3.	Student Engagement in		5
	Simulation/Demonstration/Performa		
	nceand Controls/Pre-Lab Questions.		
	Signature of Faculty (with Date):	Total Marks Obtained:	