

# DIGITAL ELECTRONICS LAB WORKSHEET

## Experiment 1.3

Visit <https://alasso.tech/>

Student Name: Alasso

Branch:

UID:

Section/Group:

Date of performance:

Subject name: Digital Electronics


### Aim:

Design a two-way switch for room light (XOR).

### Apparatus:


7400 (NAND) IC, 7402 (NOR) IC, 7486 (XOR) IC, 5V Power Supply, Breadboard, Connecting wires, Simulation software, Windows 10 PC

### Circuit diagram/ Block diagram:

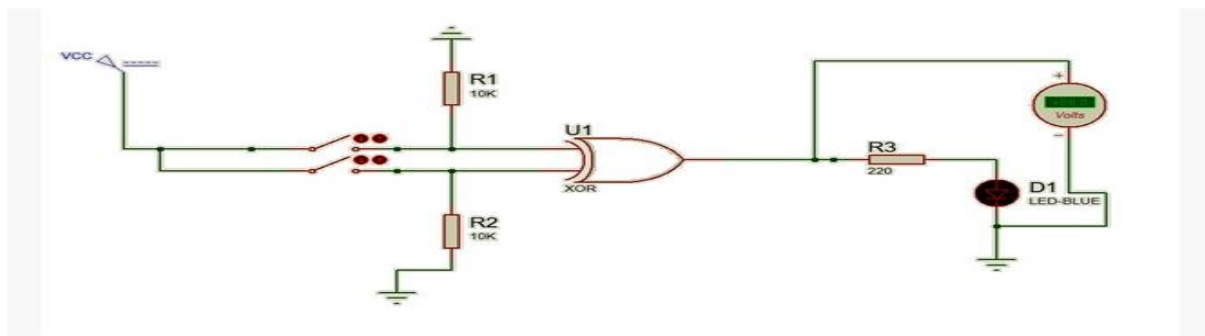

# DIGITAL ELECTRONICS LAB WORKSHEET

## Simulation Results:

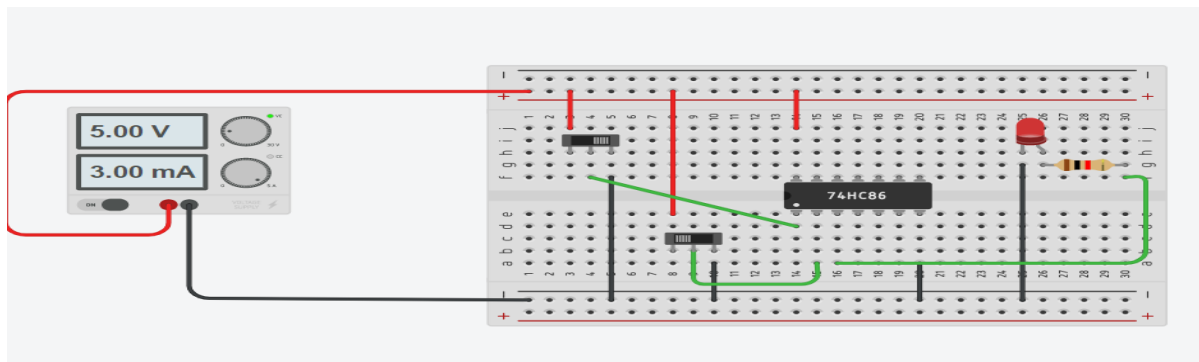

## Result

The practical applications of logic gates (NAND, NOR & XOR) were studied and implemented.

## Evaluation Grid:

Sr. No.	Parameters	Marks Obtained	Max Marks
1.	Worksheet completion including writing learning objectives/Outcomes. (To be submitted at the end of the day).		10
2.	Post Lab Quiz Result.		5
3.	Student Engagement in Simulation/Demonstration/Performance and Controls/Pre-Lab Questions.		5
	Signature of Faculty (with Date):	Total marks obtain	

